



Princess Sumaya
University
for Technology

King Abdullah II School of Engineering

EE21221

Electric Circuits (1)

Section #3

Quiz #2

Wednesday 17/11/2021

Name:

Q.1) Find i_8 , i_4 , i_{10} , i_{20} , v_{10} , v_4 , v_{20} , and P_{ix} in the circuit shown in Figure Q.1. [8-Points]

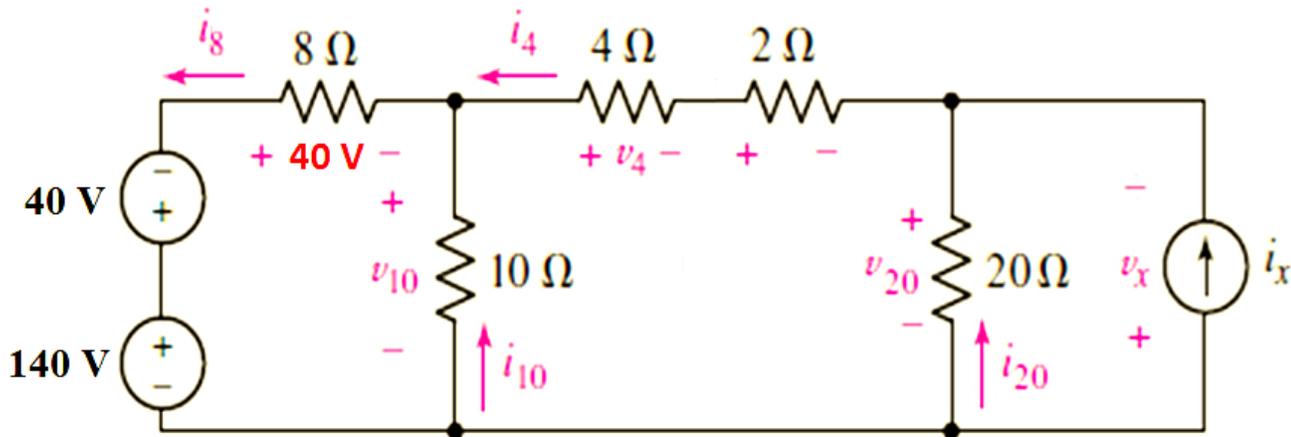


Figure Q.1

Solution:

$i_8 =$

$i_4 =$

$i_{10} =$

$i_{20} =$

$v_{10} =$


$v_4 =$

$v_{20} =$

$P_{ix} =$

Q1) * Ohm's Law

$$i_8 = \frac{-40}{8} = -5A$$

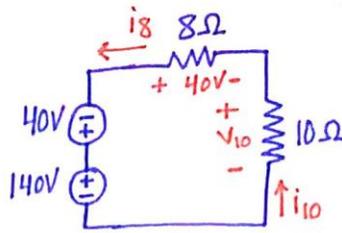

* KVL

$$-140 + 40 + 40 + V_{10} = 0$$

$$V_{10} = 60V$$

$$i_{10} = \frac{-60}{10} = -6A$$



* KCL

$$i_4 + (-6) - (-5) = 0$$

$$i_4 = 1A$$

$$V_4 = -i_4 * 4\Omega = -4V$$

$$V_{2\Omega} = -1 * 2\Omega = -2V$$

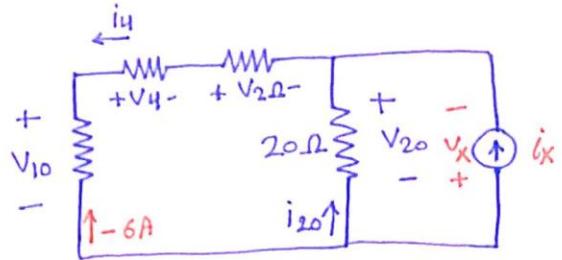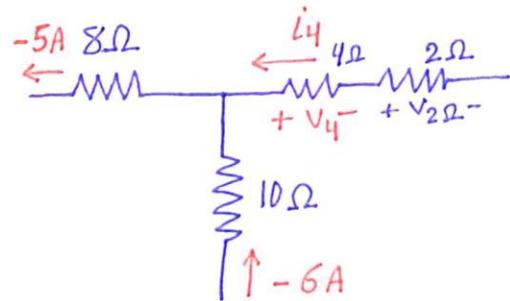


* KVL

$$-V_{10} + V_4 + V_2 + V_{20} = 0$$

$$V_{20} = 60 - (-4) - (-2) = 66V$$

$$i_{20} = \frac{-66}{20} = -3.3A$$

$$V_x = -V_{20} = -66V$$

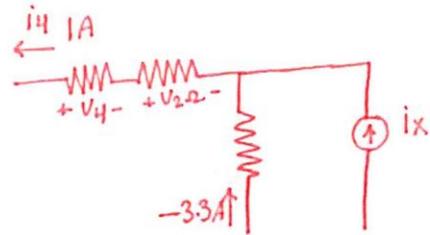

* KCL

$$i_x + (-3.3) - (1) = 0$$

$$i_x = 4.3A$$

$$P_{i_x, abs} = -(66) * (4.3) = \ominus 283.8W$$

↓
Supply

Q.2) In the circuit shown in Figure Q.2, find v_2 . [2-Points]

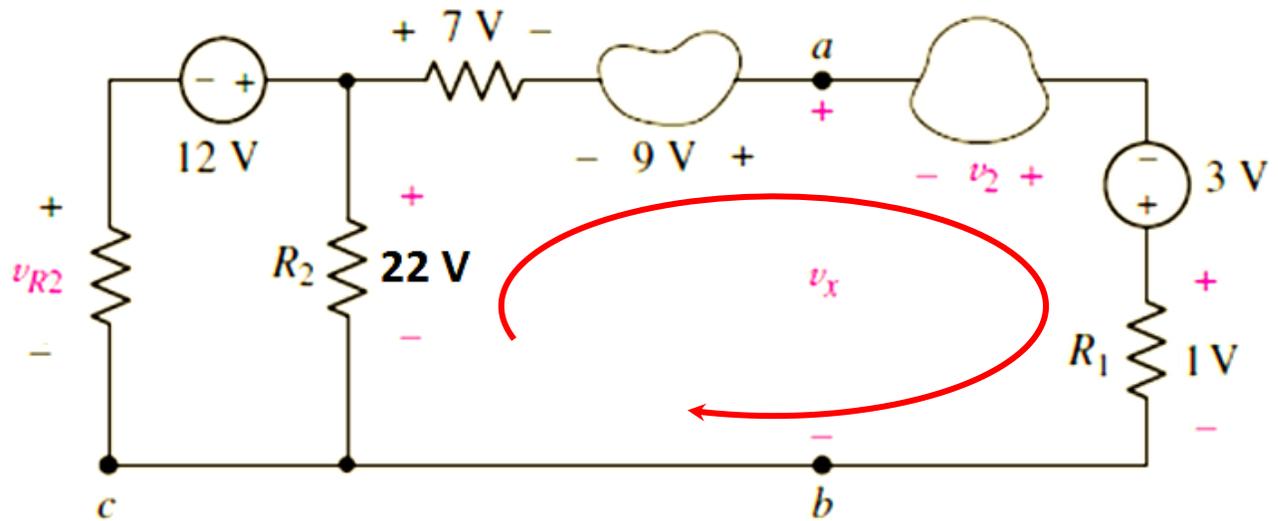


Figure Q.2

Solution:

$$v_2 = \boxed{-26 \text{ V}}$$

KVL :

$$-22 + 7 - 9 - v_2 - 3 + 1 = 0 \Rightarrow -v_2 - 26 = 0 \Rightarrow v_2 = -26 \text{ V}$$