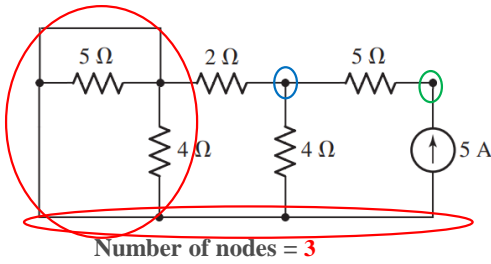



Quiz #1 Q.1

Q.1) Referring to the circuit shown in Figure Q.1, count the number of nodes: [2-Points]




1

Quiz #1 Q.2

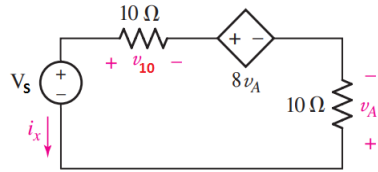Q.2) In the circuit shown in Figure Q.2, find v_{10} , v_A , and the power of the dependent source if $V_s = 100$ volts. [3-Points]

2

Quiz #1 Q.3

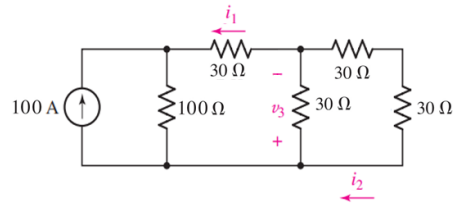Q.3) Find the current i_1 , the current i_2 , and the voltage v_3 in the circuit shown in Figure Q.3. [5-Points]

4

$$\begin{aligned}
 +100 + v_A - 8v_A + 10i_x &= 0 \\
 100 - 7v_A + 10i_x &= 0 \\
 100 - 70i_x + 10i_x &= 0 \quad \boxed{v_A = 10i_x} \\
 100 = 60i_x \Rightarrow i_x &= \frac{100}{60} = 1.6667 \text{ A} \\
 v_A = 10i_x &= 10(1.6667) = 16.667 \text{ V} \\
 v_{10} = -i_x(10) &= -16.667 \text{ V} \\
 P = VI &= (-8v_A)(i_x) = -222.27 \text{ W}
 \end{aligned}$$

